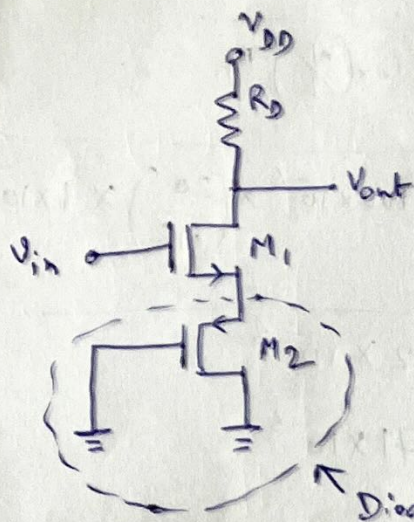
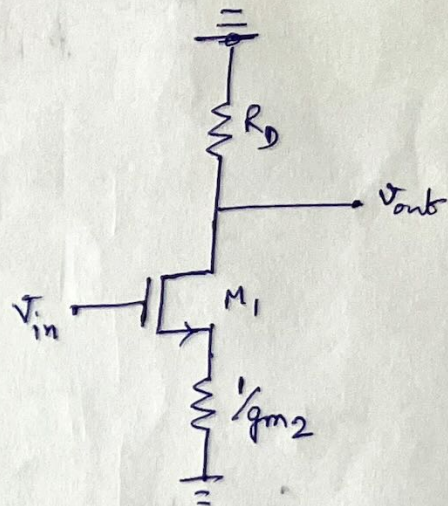
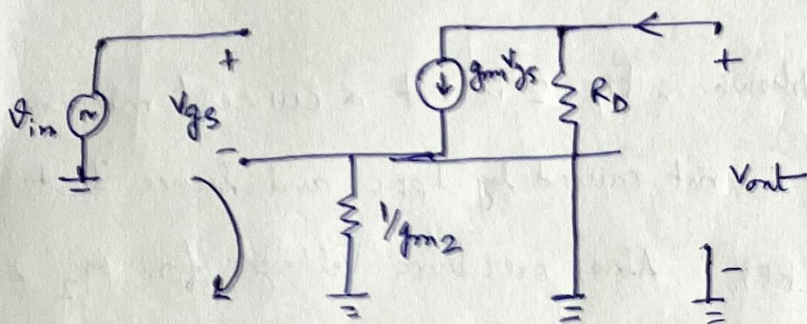


Q.1

P1

For $v=0, d=0$ Small-signal equivalent model:

Using KVL in the input loop

$$V_{in} - V_{gs} - \frac{g_{m1} V_{gs}}{g_{m2}} = 0 \quad \text{or} \quad V_{gs} = \frac{V_{in}}{\left(1 + \frac{g_{m1}}{g_{m2}}\right)}$$

$$\begin{aligned} V_{out} &= -g_{m1} V_{gs} R_D \\ &= -g_{m1} R_D \left(\frac{g_{m2} V_{in}}{(g_{m1} + g_{m2})} \right) \\ &= \frac{g_{m2} V_{in}}{g_{m1} + g_{m2}} \end{aligned}$$

$$\text{or } A_v = - \frac{g_{m1} g_{m2} R_D}{g_{m1} + g_{m2}}$$

Or, You can directly use the formula of gain for common-source stage with degenerated load.

$$A_v = - \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\text{Here, } g_{m1} = g_{m2} = \sqrt{2 \mu C_{ox} \left(\frac{W}{L} \right) I_D}$$

$$= \sqrt{2 \times 100 \times 10^{-6} \times \left(\frac{20}{.18} \right) \times 1 \times 10^{-3}}$$

$$= \sqrt{22.2 \times 10^{-6}}$$


$$= 4.71 \times 10^{-3}$$

$$\text{So, } A_v = - \frac{250 \times 4.71 \times 10^{-3} \times 4.71 \times 10^{-3}}{2 \times (4.71 \times 10^{-3})}$$

$$= -1.178$$

⑥ No, the circuit shown in Fig. 2 is not a current mirror circuit.

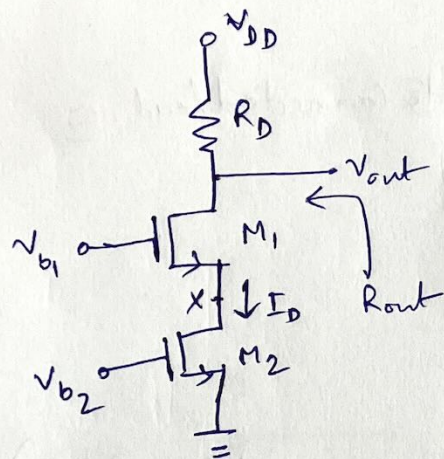Because, here V_b is not caused by I_{REF} , and hence I_{out} doesn't track I_{REF} . Also, overdrive voltage for M_2 is function of V_b which is external ~~power~~ supply voltage. Therefore I_{out} is not independent of external supply voltage.



$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \times I_D}$$

$$= \sqrt{2 \times 100 \times 10^{-6} \left(\frac{20}{0.18}\right) \times 10^{-3}}$$

$$= 4.71 \times 10^{-3}$$

for both M_1 and M_2 to be in saturation

$V_{DS1} >$ overdrive voltage of M_1

$V_{DS2} >$ overdrive voltage of M_2

$$\text{or, } V_{DS1} > V_{GS1} - V_{th1}$$

$$\geq V_{b1} - V_X - V_{th1}$$

$$\text{or, } V_{D1} > V_{b1} - V_{th1}$$

$$r_{o1} = \frac{1}{\lambda_1 I_D} = r_{o2}$$

$$= \frac{1}{0.1 \times 10^{-3}}$$

$$= 10^4$$

Therefore, the highest allowable value of V_{b1}


should be, $V_{b1} = V_{D1} + V_{th1}$

$$V_{D1} = V_{DD} - I_D R_D$$

$$= 1.8 - (1 \text{ mA} \times 500 \Omega)$$

$$= 1.3 \text{ V}$$
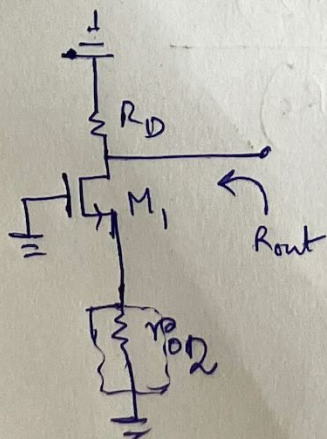
$$\therefore V_{b1} = (1.3 + 0.4) \text{ V} = 1.7 \text{ V}$$



$$R_{out} = \left\{ (1 + g_{m1} r_{o1}) r_{o2} + r_{o1} \right\} \parallel R_D$$


$$\approx g_{m1} r_{o1} r_{o2} \parallel R_D$$

$$\approx R_D$$


$$= 500 \Omega$$

Q.3

P.4

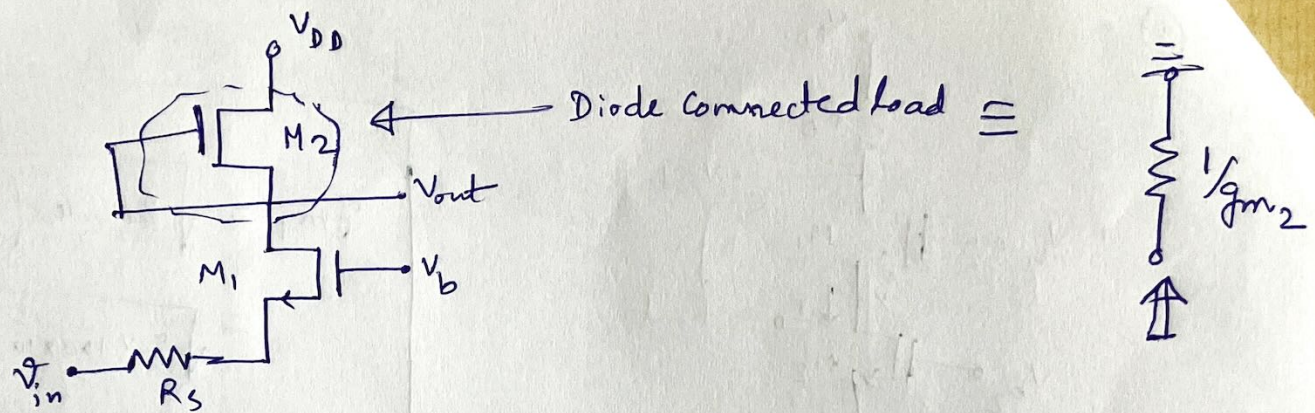

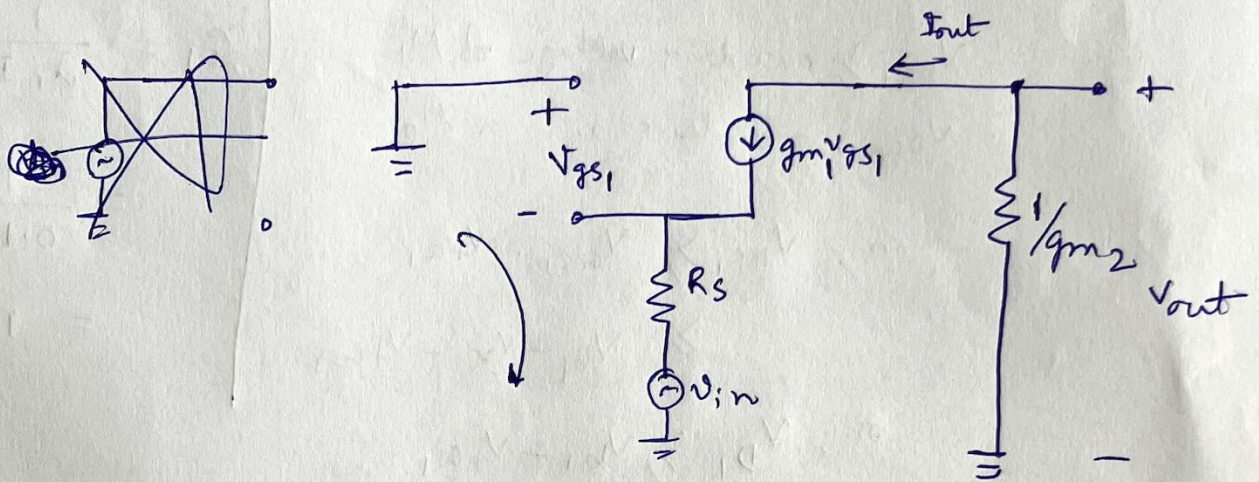(a) Small signal equivalent Model (Assuming $\lambda = 0, \gamma = 0$)



(b) Using KVL in the i/p loop

$$-V_{gs1} - R_S g_{m1} V_{gs1} - V_{in} = 0$$

$$\text{or } V_{in} = -V_{gs1} (R_S g_{m1} + 1)$$



Whereas,

$$V_{out} = -g_{m1} V_{gs1} \times \left(\frac{1}{g_{m2}} \right)$$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = \frac{+ (g_{m1} / g_{m2})}{(1 + g_{m1} R_S)}$$

(a)



This is a Cascode amplifier

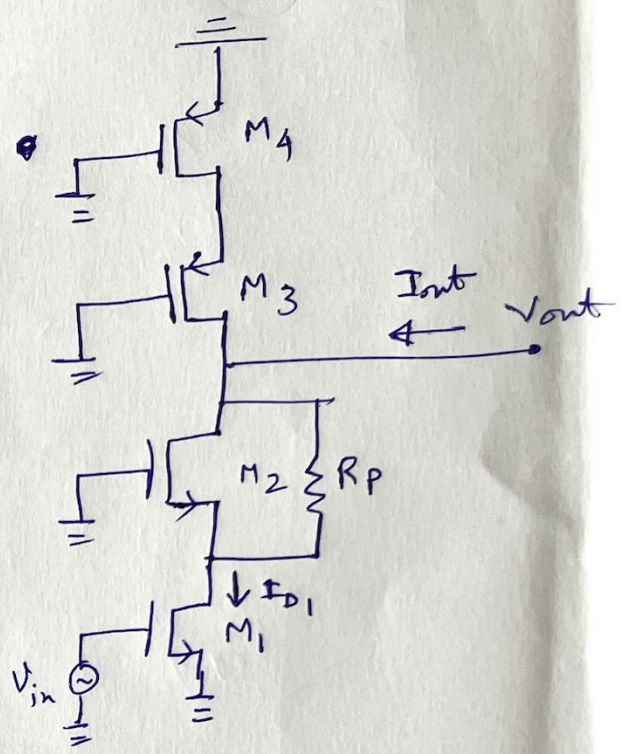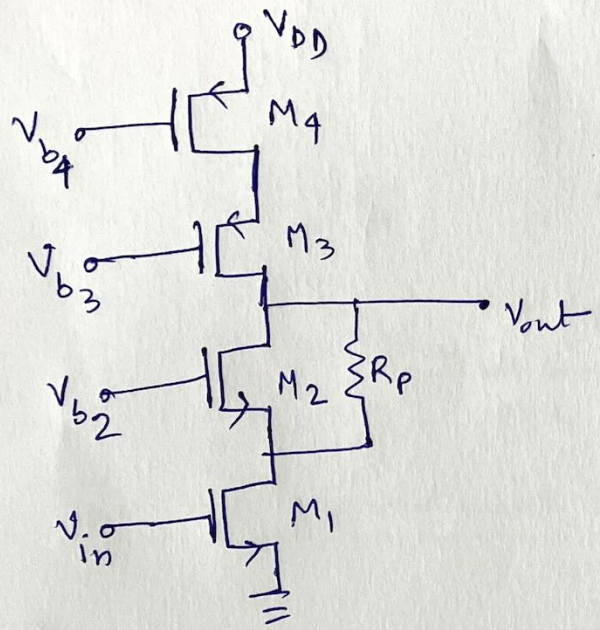

$$I_{out} = g_{m1} v_{in}$$

$$\therefore G_m = \frac{I_{out}}{v_{in}} = g_{m1}$$

R_{out} :

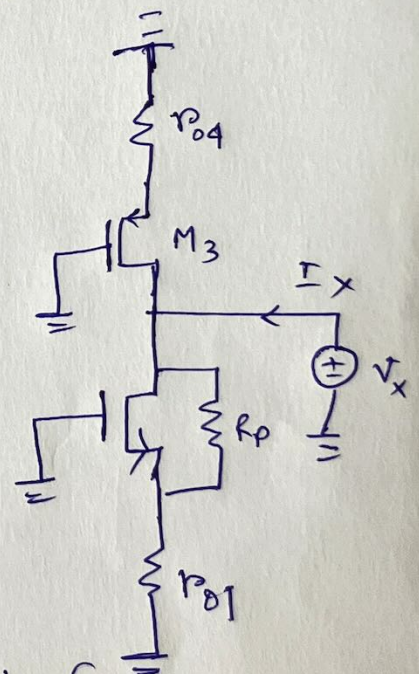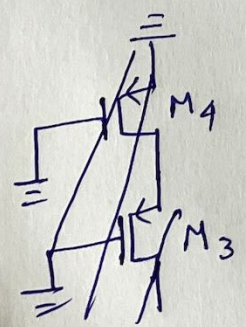

Assuming $g_m r_o \gg 1$,

$$\therefore R_{out} = \left\{ g_{m2} (r_{o2} \parallel R_P) r_{o1} \right\} \parallel \left\{ g_{m3} r_{o4} r_{o3} \right\}$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} \left[g_{m3} r_{o3} r_{o4} \parallel g_{m2} (r_{o2} \parallel R_P) r_{o1} \right]$$

6 Ans: (ii)

7 Ans: (iv)