

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING  
INDRAPRASTHA INSTITUTE OF INFORMATION TECHNOLOGY DELHI

MONSOON Semester

ECE 315/ ECE515: Analog CMOS Circuit Design

2023 – 2024

Time: 1 hour

Mid-Semester Exam-Late

M.M.: 25

**Instructions:** All questions carry sufficient information. **No further information will be provided during the exam.** Please answer all parts of the same question together at the same place, not here and there.

1. For the circuit shown in Fig. 1, the bias current must be  $I_{\text{bias}} = 0.5 \text{ mA}$ . Assume  $\mu C_{\text{ox}} = 100 \mu\text{A/V}^2$ ,  $V_{\text{TH}} = 0.4 \text{ V}$ .
- (a) Neglecting channel-length modulation, compute the required value of  $V_{b2}$  for both the transistors to be in saturation. [3+3]
- (b) What is the minimum tolerable value of  $V_{b1}$  if  $M_2$  must remain in saturation?

 


Fig. 1

 


Fig. 2

2. (a) Calculate  $I_{\text{copy}}$  for the circuit shown in Fig. 2. Assume all of the transistors operate in saturation.
- (b) Calculate the small voltage gain of the circuit shown in Fig. 3. Assume  $\lambda = 0$  for  $M_1$  and  $M_3$  but  $\lambda \neq 0$  for  $M_2$ . Also assume  $\gamma = 0$  for all the transistors. [3+4]

 


Fig. 3

 


Fig. 4

3. (a) Assuming all the MOSFETs in Fig. 4 are in saturation and  $\lambda \neq 0$ ,  $\gamma = 0$ , calculate the small-signal voltage gain of the circuit. [5+1+1]
- (b) Why do current mirrors usually employ same length for the transistors in its circuit? Explain briefly in 2-3 sentences.
- (c) Out of the following four single-stage MOS amplifiers with resistive loads, which one gives the voltage gain less than unity?
- (i) common-source, (ii) common-gate, (iii) common-drain, (iv) common-source with source degeneration

4. (a) Determine the output impedance of the stage shown in Fig. 5. Assume all of the transistors operate in saturation,  $\lambda \neq 0$ ,  $\gamma = 0$  and  $g_m r_o \gg 1$ . [4]

 


Fig. 5