

Q.1

(a) As  $\lambda = 0, \gamma = 0$

$$R_{out} = R_D = 500\Omega$$

(b) For saturation,  $V_{DS} \geq V_{GS} - V_{th}$

[As Current is maximum when the transistor operates in saturation]

$$V_{DS} \geq V_{DD} - V_{th} \geq 1.4V$$

$$\therefore I_{Dmax} = \frac{V_{DD} - V_{DS}}{R_D} = \frac{(1.8 - 1.4)V}{5k} \\ = .8mA$$

(c) The input impedance  $= 50\Omega = \frac{1}{g_m}$

$$\therefore g_m = \frac{1}{50}$$


$$g_m = \sqrt{2 \times \mu C_{ox} (W/L) I_D}$$

$$\text{on } \frac{W}{L} = \frac{g_m^2}{2 \mu C_{ox} (I_D)} = \frac{1 \times 10^{-6} \times 10^3}{50 \times 50 \times 2 \times 200 \times 0.8} \\ = \frac{10^9}{8} = 1250$$

(d) Voltage gain  $= g_m R_D = \frac{1 \times 500}{50} = 10$


of this Common gate Amplifier

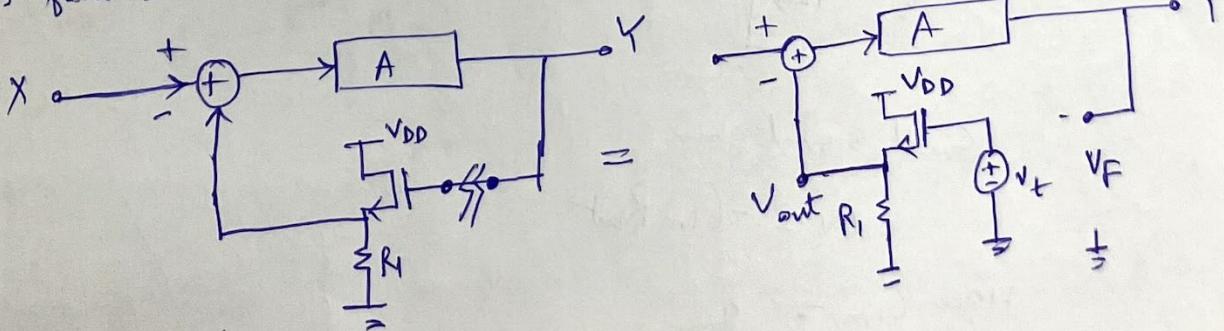Q.2 (a) After setting the main ac if to zero, breaking the loop and injecting a test signal, the ckt. in fig. 2 will look as follows —



P2

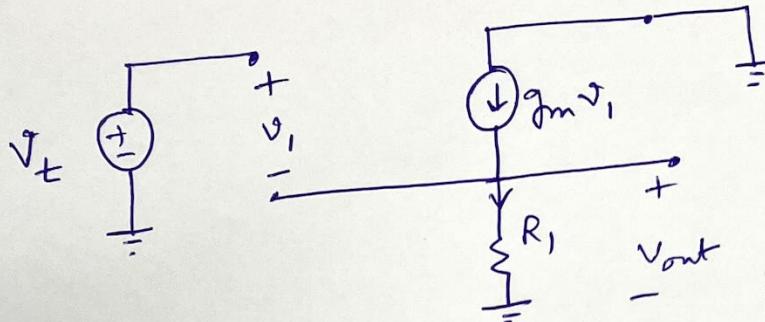As  $\lambda = 0, \gamma = 0$ , the gain of the source-follower stage can be found using



Using KCL,

$$g_m V_i = \frac{V_{out}}{R_1}$$

$$\text{or } V_i = \frac{V_{out}}{g_m R_1}$$

Using KVL,  $V_t = V_i + V_{out}$

$$= \frac{V_{out}}{g_m R_1} + V_{out}$$

$$= V_{out} \left( 1 + \frac{1}{g_m R_1} \right)$$


$$= V_{out} \left( \frac{g_m R_1 + 1}{g_m R_1} \right)$$

$$\therefore V_{out} = V_t \left( \frac{g_m R_1}{g_m R_1 + 1} \right)$$

$$\text{or } V_F = -A \left( \frac{g_m R_1}{1 + g_m R_1} \right) V_t$$

$$\boxed{-\frac{V_F}{V_t} = \text{loop gain} = + \frac{A g_m R_1}{1 + g_m R_1}}$$

(b)

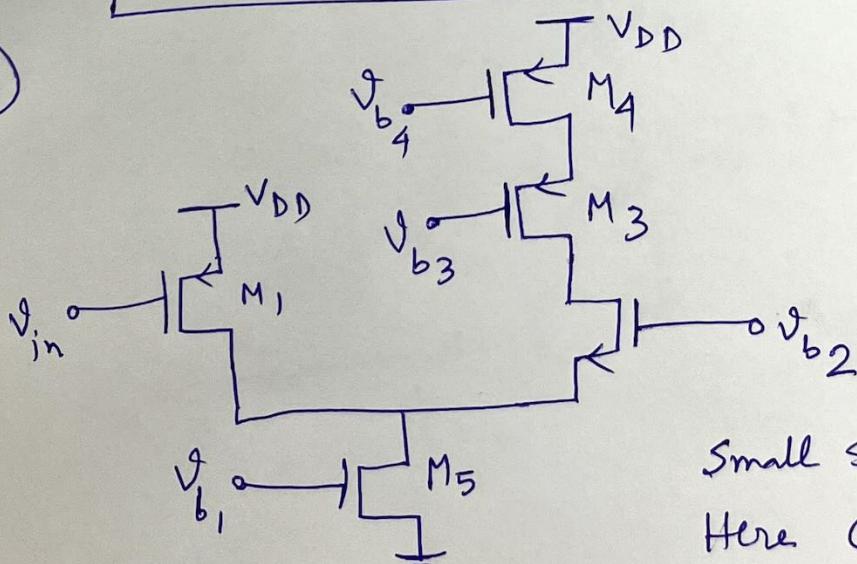


$$\boxed{\text{given } \lambda \neq 0 \\ \gamma = 0}$$

Small signal gain  $A_v = -G_m R_{out}$   
Here  $G_m \approx g_m$

For  $R_{out}$ , the circuit will appear as

P<sub>3</sub>

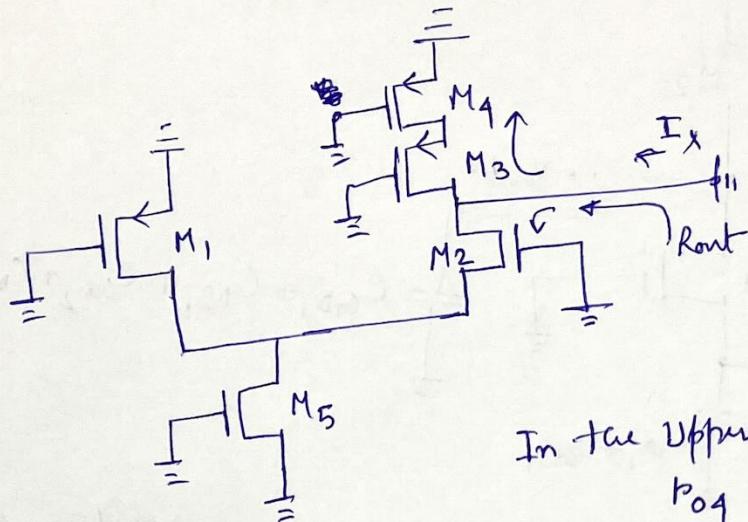

In the upper half,  $M_3$  is degenerated by  $r_{o4}$

$$\therefore R_{out, \text{upper}} = \left\{ (1 + g_m r_{o3}) r_{o4} + r_{o3} \right\}$$

In the lower half,  $M_2$  is degenerated by  $(r_{o5} || r_{o1})$

$$\therefore R_{out, \text{lower}} = \left\{ (1 + g_m r_{o2}) (r_{o5} || r_{o1}) \right\} + r_{o2}$$


$$\approx (g_m r_{o2}) (r_{o5} || r_{o1})$$


$$R_{out} = R_{out, \text{upper}} || R_{out, \text{lower}}$$

$$= (g_m r_{o3} r_{o4}) || [(g_m r_{o2}) (r_{o5} || r_{o1})]$$

$$\therefore A_v = -g_m \left[ (g_m r_{o3} r_{o4}) || [(g_m r_{o2}) (r_{o5} || r_{o1})] \right]$$

Q. 3

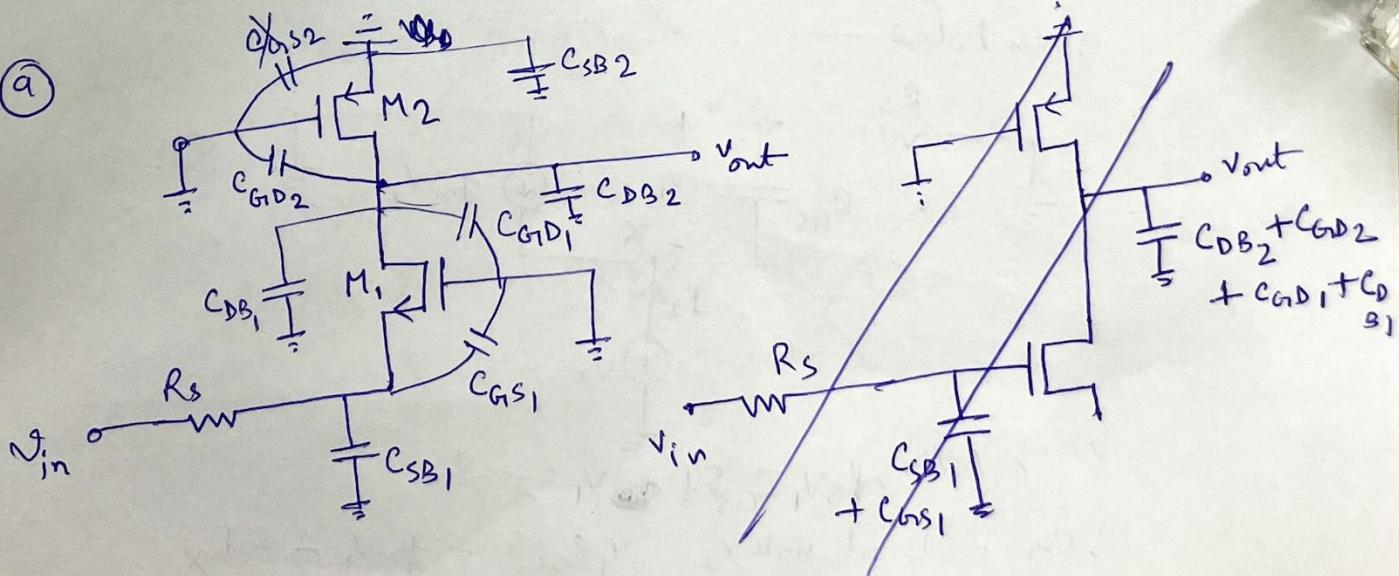

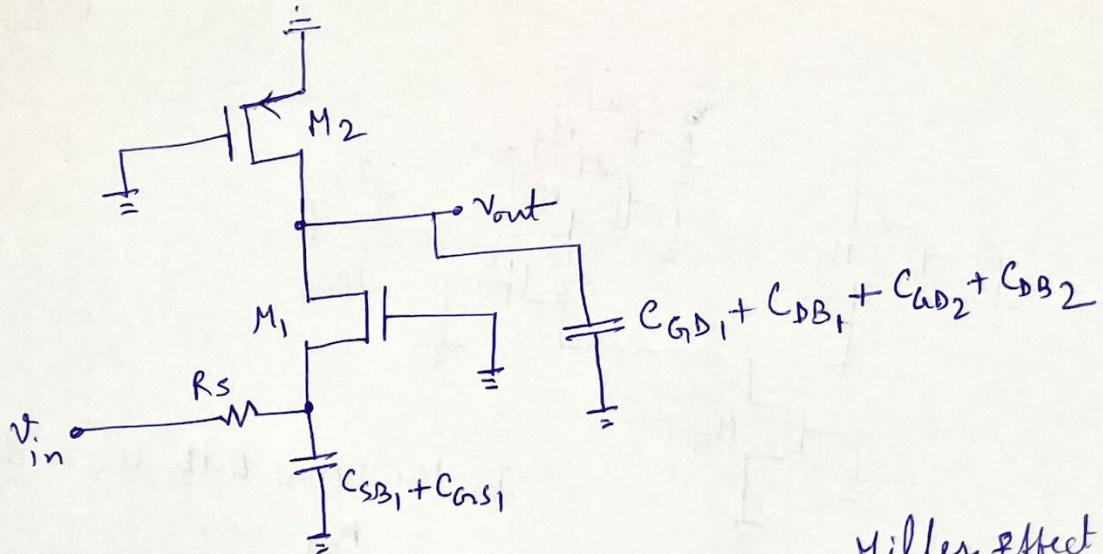

There is no capacitor which experiences Miller effect.

There are two nodes with two poles

$$\omega_{pin} = \frac{1}{(R_s \parallel \frac{1}{g_{m1}})(C_{SBD1} + C_{AGS1})}$$


[As  $\lambda = 0, \gamma = 0$  for M<sub>1</sub>  
 $\lambda \neq 0, \gamma = 0$  for M<sub>2</sub>,  
and  $g_m n_o \gg 1$ ]

$$\omega_{pout} = \frac{1}{R_o2 (C_{G,D1} + C_{D,B1} + C_{C,D2} + C_{D,B2})}$$

④ (a) To operate in deep triode region, the NMOS should have

$$V_{GS} > V_{TH} \text{ but } V_{DS} \ll 2(V_{GS} - V_{TH})$$

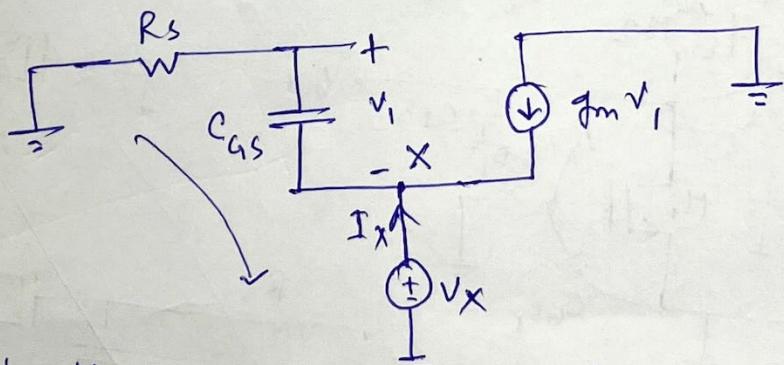(b) The equivalent circuit to find out the o/p impedance is given below —





Using KVL,  $R_s V_i + C_{GS} S + V_i = -V_X$

Using KCL at node X,  $V_i C_{GS} S + g_m V_i = -I_X$


P5

$$\therefore Z_{out} = \frac{V_x}{I_x} = \frac{R_s C_{GS} s + 1}{g_m + C_{GS} s}$$

(c)

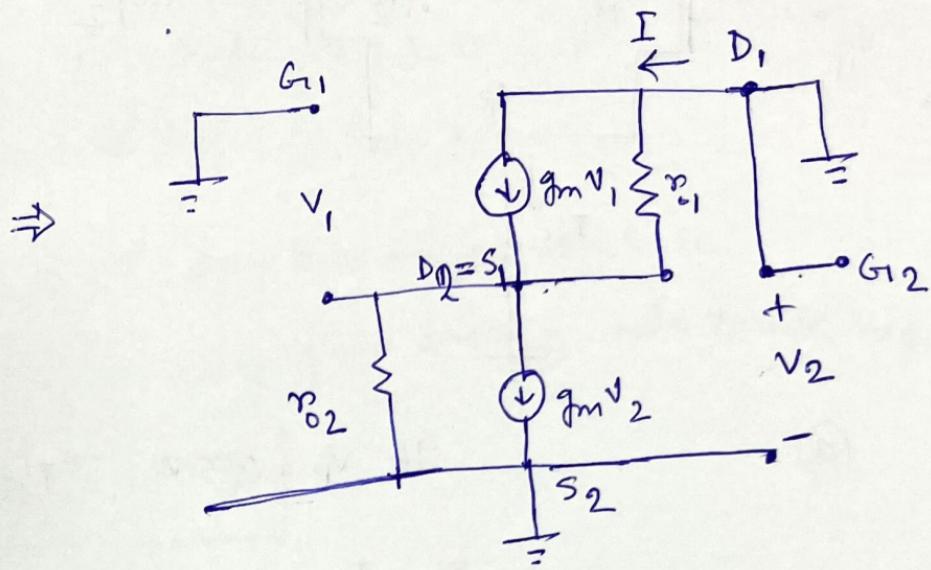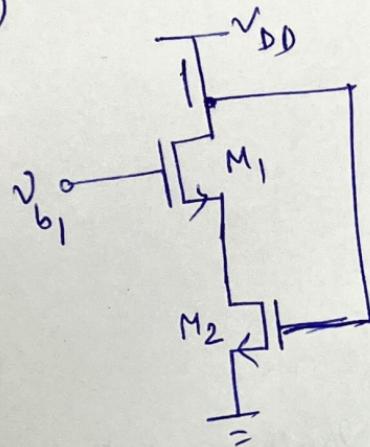

(5)

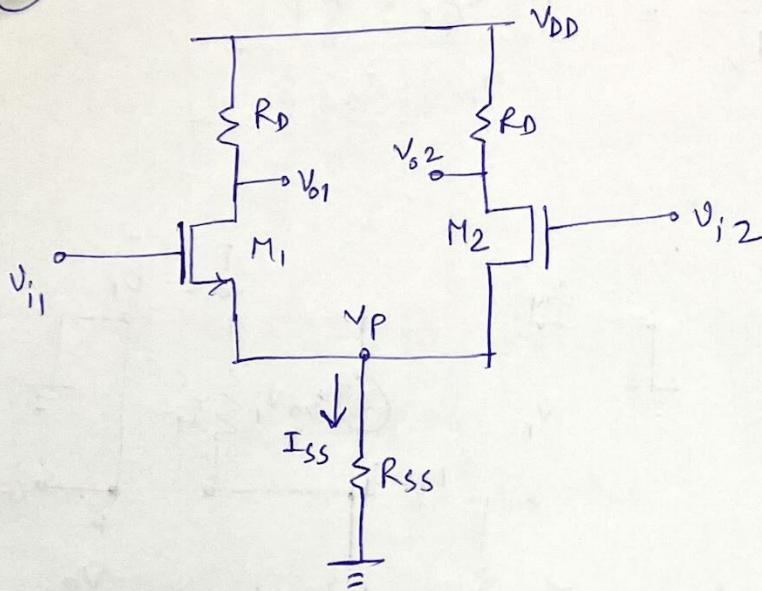

(a) If  $v_P = 0.5V$ ,  $I_{SS} = \frac{v_P - 0}{R_{SS}} = \frac{0.5V}{0.5k\Omega} = 1mA$

$$\therefore I_{D1} = I_{D2} = 0.5mA$$

$$\begin{aligned} V_{GS1} &= V_{GS2} = \sqrt{\frac{2I_{D1}}{\mu n C_{ox}(W/L)}} + V_{TH} \\ &= \sqrt{\frac{2 \times 0.5mA}{50 \mu A/V^2 \left(\frac{25}{0.5}\right)}} + 0.6 \\ &= 1.23V \end{aligned}$$

$$\boxed{\therefore V_{in,CM} = V_{GS1} + 0.5V = 1.73V}$$

(b)

$$g_m = \sqrt{2\mu n C_{ox}(W/L)} I_{D1} = \sqrt{2(50)\mu A/V^2 \left(\frac{25}{0.5}\right)} \times 0.5mA = 10 \times 1.582 = 15.82$$

$$\text{or } 4 = \frac{g_m R_D}{1 + 2g_m R_{SS}}$$

Solving,  
 $R_D = 6.528k\Omega$

$$\text{For gain} = 4 = R_D g_m$$

$$R_D = \frac{4}{g_m} = \frac{4 \times 10}{1.582} = 2.528k\Omega$$

(c)

$$\begin{aligned} V_{DS} &= V_{DD} - I_D R_D = 3 - 0.5mA \times 2.528k\Omega \\ &= (3 - 1.264)V = 1.736V \end{aligned}$$

~~$V_{DS}$  should be  $\geq V_{GS} - V_{in}$  for saturation~~


$V_{DS}$  should be  $\geq V_{GS} - V_{th}$  to stay in saturation.

$$\text{Therefore } V_{GS} \leq V_{DS} + V_{th} \\ \leq (1.736 + 0.6)V$$

$$V_{GS} \text{ should be} \leq 2.336V$$

$V_{in,M} = 1.73V$  has been used which is  $(2.336 - 1.73)V$  away from entering into triode region  
 $= 0.606V$  away

⑥ a)

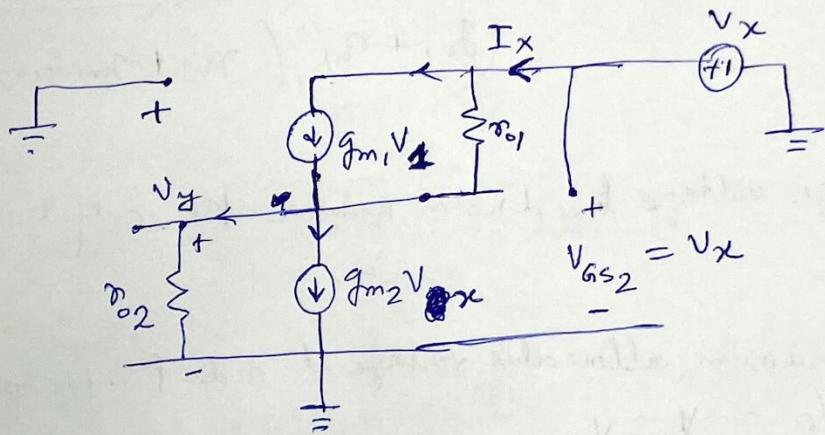

$$I_x = g_{m2} V_x + \frac{V_y}{r_{02}} \quad [ \text{Using KCL at node 2} ] \quad (1)$$

~~$V_y = R_{01} I_x - V_x$~~

$$\text{Again, } I_x = g_{m1} (-V_y) + \frac{(V_x - V_y)}{r_{01}} \quad (2)$$

$$I_x = -g_{m1} V_y + (V_x - V_y)/r_{01}$$

or  $V_y = (V_x - g_{m1} r_{01} I_x) / (1 + g_{m1} r_{01})$

Putting  $V_y$  in (1), we get

$$I_x = g_{m2} V_x + \frac{1}{r_{02}} \left( \frac{V_x r_{01} - I_x r_{01}}{1 + g_{m1} r_{01}} \right)$$

Solving for  $V_x/I_x$ , we get

$$R_{out} = [(1+g_m r_{o1})r_{o2} + r_{o1}] / [g_m r_{o2}(1+g_m r_{o1})]$$

- (b) Disadvantage: Large voltage head room reduces the output voltage swing
- (c) Minimum allowable voltage at node P to operate all Mos in sat
- $$\begin{aligned} V_p &= V_N - V_{TH} \\ &= V_{GS0} + V_{GS1} - V_{TH} \\ &= (V_{GS0} - V_{TH}) + (V_{GS1} - V_{TH}) + V_{TH} \\ &= \text{Two } \overset{\text{overdrive}}{\cancel{\text{threshold}}} \text{ voltage} + \text{one threshold voltage} \end{aligned}$$