

VLSI Design Flow

Mid Semester Exam (8th March 2021)

Time allowed: 1 hour

Maximum Marks: 40

1.

a)

Let N functions be implemented in hardware.

Total cost = $1000 + N \cdot 400$

To meet cost constraint

$1000 + N \cdot 400 < 2500$

$N < 3.75$

Maximum $N=3$

The three functions that take maximum percentage of time are moved to dedicated hardware are: F6, F8 and F3. **2 Marks**

Cost = $1000 + 3 \cdot 400 = \text{Rs } 2200/-$ **1 Mark**

Runtime of functions implemented in software = $0.30 \cdot 1000 = 300$ s

Runtime of functions implemented using dedicated hardware = $(1/10) \cdot 0.70 \cdot 1000 = 70$ s

Total runtime = $300 + 70 = 370$ s. **2 Marks**

b) Since runtime with 3 functions moved to dedicated hardware is 370 s (more than target of below 350), we need to move more function to dedicated hardware.

Let us move 4th top function F5 to dedicated hardware that consumes 10% of total runtime.

Total runtime = $0.20 \cdot 1000 + (1/10) \cdot 0.80 \cdot 1000 = 200 + 80 = 280$ s.


So we need to move F6, F8, F3, and F5 to dedicated hardware. **2 Marks**

Runtime = 280 s **1 Mark**

Cost = $1000 + 4 \cdot 400 = \text{Rs. } 2600/-$ **2 Marks**

2.

(a)

 

Clock-frequency = 1 GHz

Time period = $10^{-9}s = 1000\text{ ps}$

Setup analysis

Path from F1 to F3:

Setup Slack: $(1000+5+50)-(5+5+50+100+30)=865\text{ ps}$ 1.5 Marks

Path from F2 to F3:

Setup Slack: $(1000+5+50)-(5+30+50+100+30)=840\text{ ps}$ 1.5 Marks

Therefore, the worst setup slack is 840 ps (F2 to F3) 1 Mark

Hold analysis

Path from F1 to F3:

Hold Slack: $(5+5+50+100)-(5+50+10)=95\text{ ps}$ 1.5 Marks


Path from F2 to F3:

Hold Slack: $(5+30+50+100)-(5+50+10)=120\text{ ps}$ 1.5 Marks


Therefore, the worst hold slack is 95 ps (F1 to F3) 1 Mark

(b)

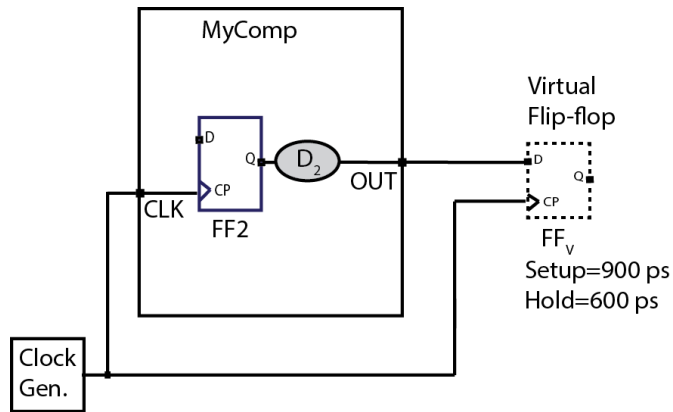The requirement is similar if we consider a flip-flop at the output port with a setup and hold times of 900 ps and 600 ps, as follows:



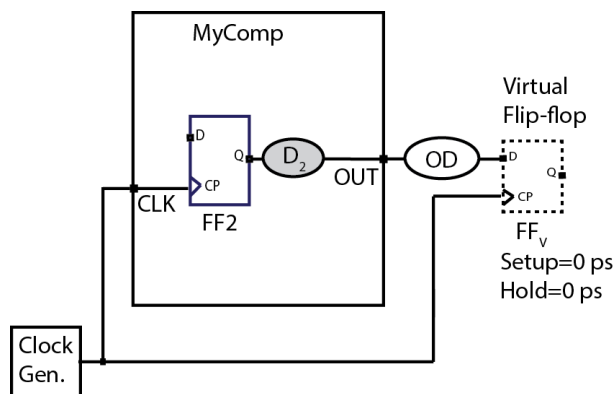This situation needs to be modelled using SDC `set_output_delay` which works as follows:



The above two figures should yield the same constraint or requirement.

To make them same, we need to find adjust the delay of the element OD for the maximum case (setup) and the minimum case (hold).

For setup analysis:

From first figure:

$$T_{FF} + T_{D2,max} + 900 < T_{period}$$

From second figure:

$$T_{FF} + T_{D2,max} + T_{OD,max} < T_{period}$$

Therefore: $T_{OD,max} = 900$ ps

1 Marks

For hold analysis:

From first figure:

$$T_{FF} + T_{D2,min} > 600$$

$$T_{FF} + T_{D2,min} - 600 > 0$$

From second figure:

$$T_{FF} + T_{D2,min} + T_{OD,min} > 0$$

Therefore: $T_{OD,min} = -600$ (Note the negative sign). 3 Marks

We need to find the value of delay

The SDCs are:

`create_clock -name SYS_CLOCK -period 2000 [get_ports CLK]` 1 Mark

`set_output_delay 900 -max -clock [get_clocks SYS_CLK] [get_ports OUT]`

`set_output_delay -600 -min -clock [get_clocks SYS_CLK] [get_ports OUT]`

2 Marks


-0.5 if -clock option is missing

3.


a)

Each of the following four miters need to be drawn separately to get marks.

 
Specifically, the inputs and instance name should be marked correctly in each miter and an XOR gate must be placed at the output.




1 Mark

 

1 Mark

 

1 Mark

 

1 Mark

b) The Miter-3 will show failure because output can be made 1. **2 Marks**

The patterns at inputs that satisfy the miter (or make the models inequivalent or fail) are:

$\$F1/Q=0,F2/Q=0\$$ and $\$F1/Q=1,F2/Q=1\$$. **3 Marks**

c) No, these are invalid patterns, because F1/D is the complement of F2/D. Therefore, the possible values of $\{F1/Q,F2/Q\}$ are $\{01\}$ and $\{10\}$. Therefore, $\{00\}$ and $\{11\}$ cannot occur. Thus, it is a false failure. **6 Marks**