

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING
INDRAPRASTHA INSTITUTE OF INFORMATION TECHNOLOGY DELHI

MONSOON Semester

ECE 315/ ECE515: Analog CMOS Circuit Design

2023 – 2024

Time: 2 hours

End-Semester Exam

M.M.: 30

Instructions: All questions carry sufficient information. **No further information will be provided during the exam.** Please answer all parts of the same question together at the same place, not here and there.

1. For the circuit shown in Fig. 1, $V_{DD} = 1.8 \text{ V}$, $R_D = 500 \Omega$ and transistor M_1 is characterized by the following parameters: $\mu C_{ox} = 200 \mu\text{A/V}^2$, $V_{TH} = 0.4 \text{ V}$, $\lambda = 0$, $\gamma = 0$. The circuit provides an input impedance of 50Ω .
 (a) What is the output resistance of the circuit? [1+1+2+1]
 (b) What is the value of maximum allowable of drain current?
 (c) Calculate the required value of W/L for the maximum allowable value of drain current.
 (d) Compute the voltage gain.

 


Fig. 1

 


Fig. 2

2. (a) Find the loop-gain of the circuit shown in Fig. 2 where A is given as open-loop gain. Assume $\lambda = 0$, $\gamma = 0$ for M_1 .
 (b) Find the small signal gain of the amplifier shown in Fig. 3. Assume $\lambda \neq 0$, $\gamma = 0$ and $g_m r_o \gg 1$ for all the transistors. [2+3]

 


Fig. 3

 


Fig. 4

3. Let us assume that the circuit in Fig. 4 is given for frequency response analysis.
 (a) Identify the capacitors, which experience Miller effect, if there is any. [2+3]
 (b) Identify the poles by inspection. Assume $\lambda = 0$, $\gamma = 0$ for M_1 , $\lambda \neq 0$, $\gamma = 0$ for M_2 and $g_m r_o \gg 1$ for all MOS devices.
4. (a) What are the usual bias conditions for the NMOS device shown in Fig. 5 to operate in deep triode region?
 (b) Neglecting all other capacitances, find the output impedance of the circuit shown in Fig. 6. Assume $\lambda = 0$, $\gamma = 0$ for the transistor and I_S is an ideal current source. [1+2+2]

 


Fig. 5

 


Fig. 6

(c) Draw the small-signal equivalent model for the circuit shown in Fig. 7 with proper labeling. Assume $\lambda \neq 0$ and $\gamma = 0$ for both the transistors.

 


Fig. 7

 


Fig. 8

5. For the circuit shown in Fig. 8, $V_{DD} = 3$ V, $R_{SS} = 500 \Omega$, $(W/L)_{1,2} = 25/0.5$, $(\mu C_{ox})_{1,2} = 50 \mu A/V^2$, $V_{TH1,2} = 0.6$ V. Assume $\lambda = 0$, $\gamma = 0$ for all the MOS devices. [2+2+1]
- What is the required input CM voltage for which V_P can be at least 0.5 V?
 - Calculate R_D for which the differential mode gain is 4.
 - Calculate the amount of voltage the transistors are away from entering the triode region.
6. (a) Calculate the output resistance (R_{out}) denoted in the circuit of Fig 7. Assume $\lambda \neq 0$ and $\gamma = 0$ for both the transistors. [2+1+2]
- (b) Give just one disadvantage of having large voltage headroom in a MOS circuit.
- (c) Assume all MOS devices in Fig. 9 are identical having threshold voltage V_{TH} , and $\lambda = 0$, $\gamma = 0$ for all of them. Find minimum allowable voltage at node P of the circuit to operate all the transistors in saturation.

 


Fig. 9