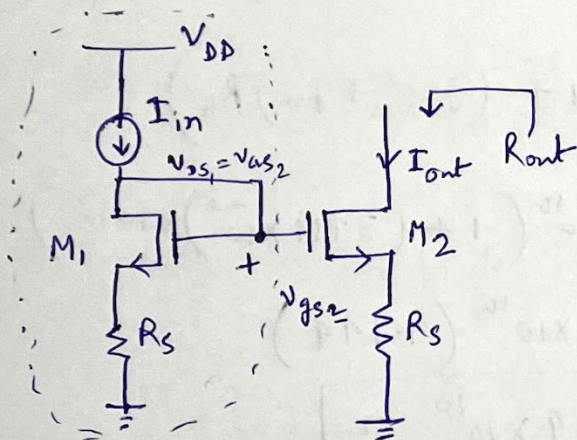


Q.1



Given, $I_{in} = 100 \mu A$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{10}{.2} = 50$$

$$R_s = 1 k\Omega$$

$$g_{mb} = 0.2 g_m$$

$$\mu_{Cox} = 110 \mu A/V^2$$

$$\lambda = 0.15 \mu m/V$$

This is a current mirror circuit and $M_1 = M_2$

Therefore $I_{out} = I_{in}$

$$r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{0.15 \times 10^{-6} \times 100 \times 10^{-6}}$$

$$= \frac{1 \times 10^{+12}}{15} \Omega$$

$$= 6.67 \times 10^{+10} \Omega$$

As the left half of the circuit appears open,

$$R_{out} = r_{o2} + \left\{ \left[1 + (g_{m2} + g_{mb2}) r_{o2} \right] R_s \right\}$$

As $(g_{m2} + g_{mb2}) r_{o2} \gg 1$

$$R_{out} \approx r_{o2} + \left\{ (g_{m2} + g_{mb2}) r_{o2} R_s \right\}$$

$$= r_{o2} \left[1 + (g_{m2} + g_{mb2}) R_s \right] \quad \text{--- (1)}$$

If someone doesn't approximate here, that's also ok.

Here $g_{m2} = \sqrt{2 \mu_{Cox} \left(\frac{W}{L}\right) I_{in}}$

$$= \sqrt{2 \times 110 \times \left(\frac{10}{.2}\right) 100 \times 10^{-12}}$$

$$= 10^{-6} \left(\sqrt{2 \times 110 \times 50 \times 100} \right)$$

$$= 1.048 \times 10^{-3} \Omega^{-1}$$

$$= 0.2096 \times 10^{-3} \text{ moh}$$

$$\therefore g_{mb2} = 0.2 \times 1.048 \times 10^{-3} \Omega^{-1} = 2.096 \times 10^{-4} \Omega^{-1}$$

Putting r_{o2} , g_{m2} and g_{mb2} and R_s in eqn. ①

$$R_{out} = r_{o2} \left(1 + (g_{mb2} + g_m) R_s \right) \Omega$$

$$= 6.67 \times 10^{10} \left(1 + \left(\frac{1.257}{3.144} \times 10^{-3} \right) \times 1 \times 10^3 \right)$$


$$= 6.67 \times 10^{10} \left(\frac{2.257}{4.144} \right)$$

$$\therefore R_{out} = \frac{26.64 \times 10^{10}}{2} \Omega$$


$$15.05 \times 10^{10} \text{ ohm}$$

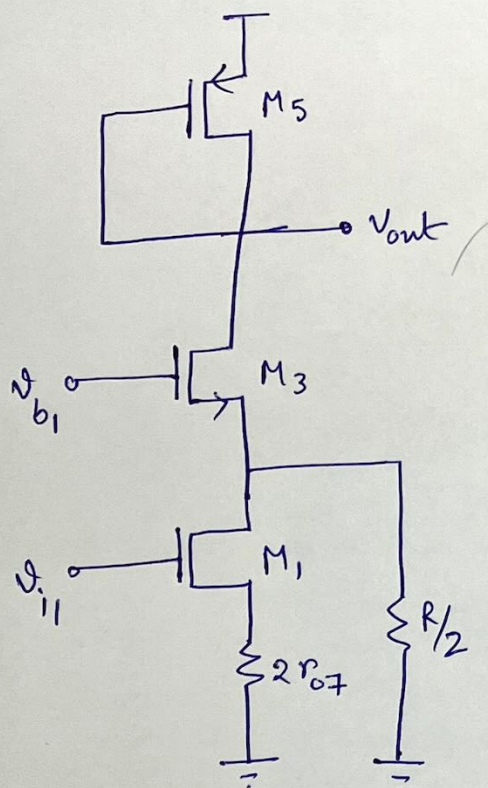Q.2

As given, assuming symmetry, we can analyse the diff. amplifier using half-circuit method. The half-circuit will be



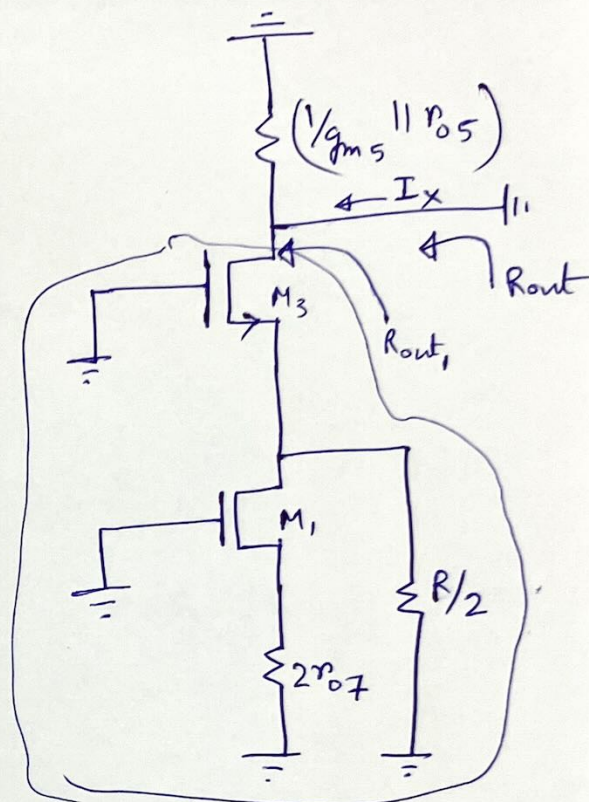For o/p resistance
the equivalent
 \Rightarrow
small signal
ckt.



$$R_{out} = \left(\frac{1}{g_{m5}} \parallel r_{o5} \right) \parallel R_{out1}$$

$$= \frac{1}{g_{m5}} \parallel R_{out1}$$

[As $g_m r_o \gg 1$ for all MOS devices]

$$R_{out1} = \left[(1 + g_{m3} r_{o3}) \cdot \left\{ R/2 \parallel \left[(1 + g_{m1} r_{o1}) 2r_{o7} + r_{o1} \right] \right\} \right] + r_{o3}$$

$$\approx \left(g_{m3} r_{o3} \cdot \frac{R}{2} \right) + r_{o3} \quad \left[\text{As } g_m r_o \gg 1 \text{ for all MOS devices} \right]$$

$$\therefore R_{out} = \frac{1}{g_{m5}} \parallel \left\{ \left(g_{m3} r_{o3} \frac{R}{2} \right) + r_{o3} \right\}$$

Q.3

(a) For single stage Source-Follower CMOS amplifier
Miller's approximation decreases the i/p capacitance.


(b) We need negative feedback (1) to desensitization the gain
from external factors.

or, (2) \rightarrow We need -ve feedback to obtain high precision.

(12)

Q.3

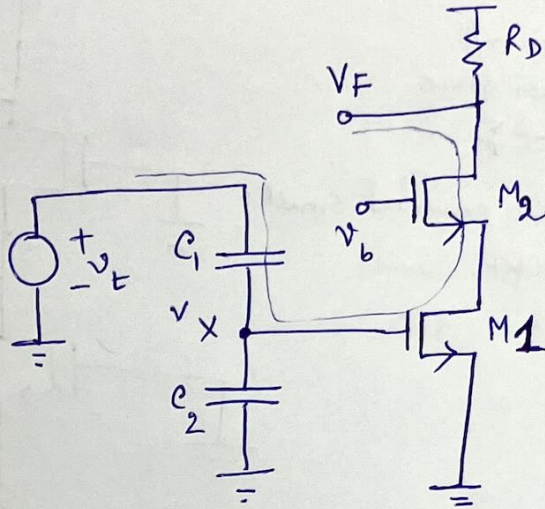- (C) After setting the main i/p (ac) to zero, breaking the loop and injecting a test signal, the circuit in Fig. 3 will look as follows —



Gain of this ckt.

$$\frac{v_F}{v_X} = -G_m R_{out}$$

$$R_{out} = R_D \parallel \left\{ (1 + g_{m2} r_{o2}) r_{o1} + r_{o2} \right\}$$

$$G_m = g_{m1}$$


$$v_X = v_t \times \left(\frac{C_1}{C_1 + C_2} \right)$$

$$v_F = -v_X \left[R_D \parallel \left\{ (1 + g_{m2} r_{o2}) r_{o1} + r_{o2} \right\} \right] g_{m1}$$


$$= -v_t \left(\frac{C_1}{C_1 + C_2} \right) \left[R_D \parallel \left\{ (1 + g_{m2} r_{o2}) r_{o1} + r_{o2} \right\} \right] g_{m1}$$

$$\therefore \text{Loop Gain} = \frac{v_F}{v_t} = \left(\frac{C_1}{C_1 + C_2} \right) \left[R_D \parallel \left\{ (1 + g_{m2} r_{o2}) r_{o1} + r_{o2} \right\} \right] g_{m1}$$

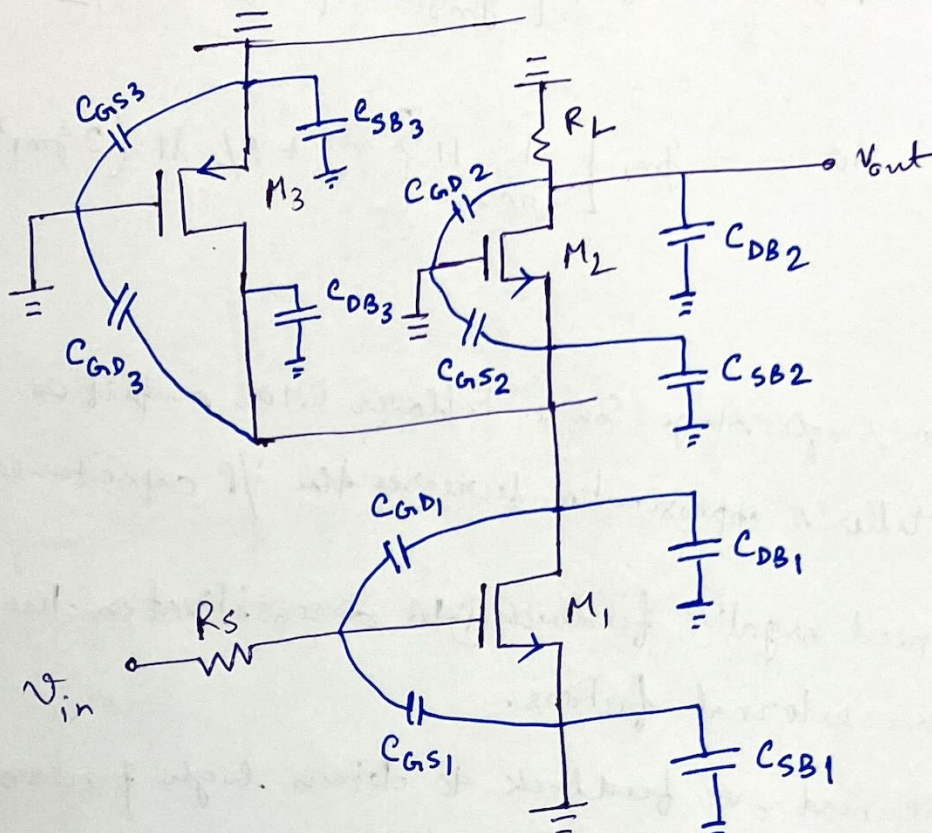If we draw all the capacitances for fig. 4, we get
and ground the independent dc sources.



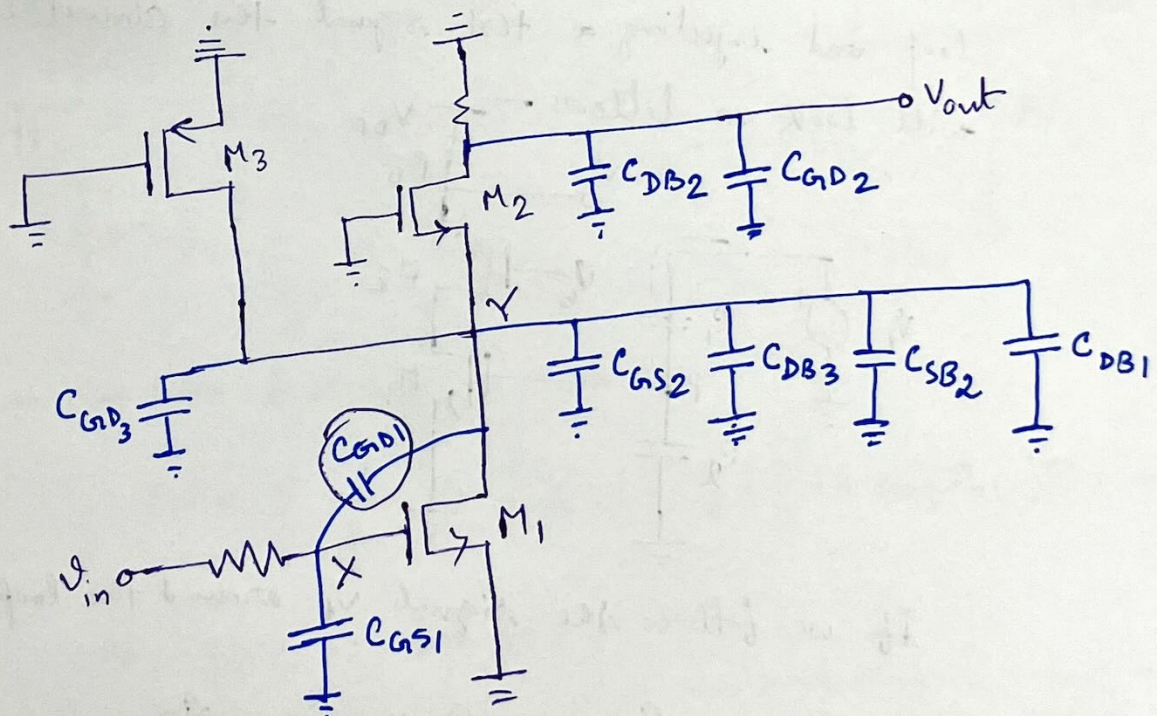Removing and merging the capacitances, we get



Here C_{GD1} only experiences Miller effect.
There are three poles, which are —

$$\omega_{p_x} = \frac{1}{R_s \left(C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2}} \right) C_{GD1} \right)}$$

Because $A_v = - \frac{g_{m1}}{g_{m2}}$ (Considering $\gamma=0$ & $\lambda=0$)

for all MOS devices, as given)

$$\omega_{p_y} = \frac{1}{\frac{1}{g_{m2}} \left[C_{DB1} + C_{DB3} + C_{GS2} + C_{SB2} + \left(1 + \frac{g_{m2}}{g_m} \right) C_{GD1} \right]}$$

$$\omega_{p_{out}} = \frac{1}{R_L \left(C_{DB2} + C_{GD2} \right)}$$