 




Differential and Multistage Amplifier

CHAPTER 7

Differential and Multistage Amplifiers



Chapter 7 Differential and Multistage Amplifiers

7.1 The MOS Differential Pair

7.2 Small-Signal Operation of the MOS Differential Pair

7.3 The BJT Differential Pair


7.4 Other Nonideal Characteristics of the Differential Amplifier

7.5 The Differential Amplifier with Active Load

7.6 Frequency Response of the Differential Amplifier

7.7 Multistage Amplifiers

Introduction to multistage amplifiers

 


Configuration of multistage voltage op amp


Input (or first) stage

- ① Provide gain
- ② Provide a high input resistance to avoid signal loss
- ③ Use differential pair to increase CMRR

Infinite input impedance

 


Introduction to multistage amplifiers

 


Configuration of multistage voltage op amp

Middle stage

 - ① Provide large gain
- ② Convert the differential to single signal
- ③ Shift the dc level of the signal to increase the output swing



Introduction to multistage amplifiers

 

Configuration of multistage voltage op amp

Output stage

- ① Provide low output resistance to avoid gain loss
- ② Supply the required current to the load

Zero output impedance

$$V_{load} = A(v_2 - v_1) \frac{Z_{load}}{Z_{out} + Z_{load}} = A(v_2 - v_1) (Z_{out} \ll Z_{load} \rightarrow Z_{out} = 0)$$

7.7.1 A Two-Stage CMOS Op Amp

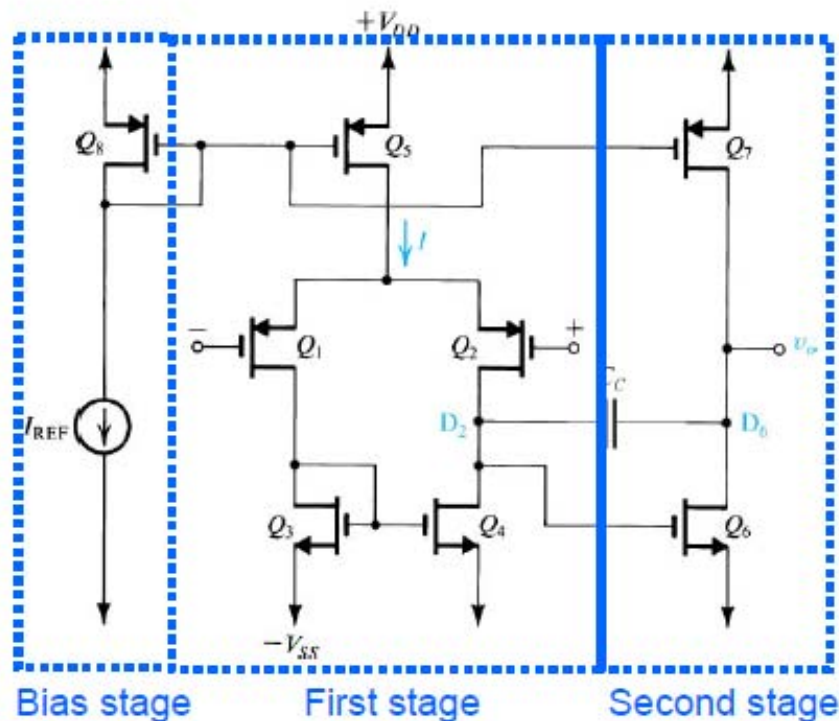


Figure 7.40 Two-stage CMOS op-amp configuration common source Amp.

Configuration of two stage amplifier

Bias stage

- ① Reference bias current: I_{REF}
- ② Q_8 and Q_5 : current mirror

First stage

- ① Q_1 and Q_2 : input differential pair
- ② Q_3 and Q_4 : active load

Second stage

- ① Q_6 : input
- ② Q_7 : current source load
- ③ C_c : frequency compensation capacitor (Ch. 8 & 9)

7.7.1 A Two-Stage CMOS Op Amp

 


Figure 7.40 Two-stage CMOS op-amp configuration.

Find the voltage gain of two stage amplifier

The voltage gain of the first stage

$$\textcircled{1} A_1 = -g_{m1}(r_{o2} \parallel r_{o4}) \quad (7.197)$$

The voltage gain of the second stage

$$\textcircled{1} A_2 = -g_{m6}(r_{o6} \parallel r_{o7}) \quad (7.198)$$

The voltage gain of two stage amplifier

$$\textcircled{1} A_{dc} = A_1 A_2 = g_{m1} g_{m6} (r_{o2} \parallel r_{o4}) (r_{o6} \parallel r_{o7}) \quad (7.199)$$

- This circuit does not have a low-output resistance stage ($r_{o6} \parallel r_{o7}$), nevertheless, the circuit is very popular in implementing op-amps in VLSI circuit, where the op-amp needs to drive only a small capacitive load.

Example 7.3

	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8
W/L	20/0.8	20/0.8	5/0.8	5/0.8	40/0.8	10/0.8	40/0.8	40/0.8

 


Figure 7.40 Two-stage CMOS op-amp configuration.

Conditions

$$I_{REF} = 90 \mu A, V_m = 0.7 V, V_{tp} = -0.8 V, \mu_n C_{ox} = 160 \mu A/V$$

$$\mu_p C_{ox} = 40 \mu A/V^2, |V_A| = 10 V, V_{DD} = V_{SS} = 2.5 V$$

Solution

① Since $(W/L)_5 = (W/L)_7 = (W/L)_8$, $I = I_{REF}$

② Drain current of each device

$$I_D = \frac{1}{2} (\mu C_{ox}) (W/L) V_{OV}^2$$

③ Thus, the overdrive voltage, the transconductance, and the output resistance of each device

$$V_{ov} = \sqrt{\frac{2I_D}{\mu C_{ox} (W/L)}}, |V_{GS}| = |V_t| + |V_{OV}|, g_m = \frac{2I_D}{|V_{OV}|}, r_o = |V_A|/I_D$$

Example 7.3

Table 7.1	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8
$I_D(\mu\text{A})$	45	45	45	45	90	90	90	90
$V_{OV}(\text{V})$	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3
$V_{GS}(\text{V})$	1.1	1.1	1	1	1.1	1	1.1	1.1
g_m	0.3	0.3	0.3	0.3	0.6	0.6	0.6	0.6
r_o	222	222	222	222	111	111	111	111

- ① Voltage gain of 1st stage & 2nd stage

$$A_1 = -g_{m1}(r_{o2} \parallel r_{o4}) = -33.3\text{V/V}$$

$$A_2 = -g_{m6}(r_{o6} \parallel r_{o7}) = -33.3\text{V/V}$$

- ② Overall open-loop dc gain

$$A_0 = A_1 A_2 = (-33.3) \times (-33.3) = 1109\text{V/V}$$

$$A_0(\text{dB}) = 20\log 1109 = 61\text{dB}$$

Example 7.3

- ③ Lower limit of the input common-mode range;

$$V_{ICM,min} = -V_{SS} + V_{GS3} - |V_{tp}| = -2.5 + 1 - 0.8 = -2.3V$$

- ④ Upper limit of the input common-mode range;


$$V_{ICM,max} = V_{DD} - V_{OV5} - V_{SG1} = 2.5 - 0.3 - 1.1 = 1.1V$$

- ⑤ Highest allowable output voltage;

$$V_{O,max} = V_{DD} - |V_{OV7}| = 2.5 - 0.3 = 2.2V$$

- ⑥ Lowest allowable output voltage;
 
$$V_{O,min} = -V_{SS} + V_{OV6} = -2.5 + 0.3 = -2.2V$$



7.7.1 A Two-Stage CMOS Op Amp

 


Figure 7.40 Two-stage CMOS op-amp configuration.

Systematic offset (not random offset)

- ① Two input terminals: grounded
- ② If the input stage is perfectly matched
 $V_{D3} = V_{D4} = -V_{SS} + V_{GS4}$
 $V_{GS4} = V_{GS6}$

- ③ Thus, drain current through Q6

$$I_6 = \frac{(W/L)_6}{(W/L)_4} (I/2)$$

- ④ And drain current through Q7

$$I_7 = \frac{(W/L)_7}{(W/L)_5} I$$


- ⑤ For no offset, $I_6 = I_7$

$$\frac{(W/L)_6}{(W/L)_4} = 2 \frac{(W/L)_7}{(W/L)_5}$$

$$(W/L)_4 = 5/0.8, (W/L)_6 = 10/0.8$$

$$(W/L)_5 = 40/0.8, (W/L)_7 = 40/0.8$$

7.7.1 A Two-Stage CMOS Op Amp

 

A bias circuit that stabilizes g_m

- ① Independent of supply voltage
- ② Independent of MOSFET threshold voltage
- ③ Determined only by a single resistor and the device dimensions

Generally, R_B is an off-chip resistor.

Figure 7.42 Bias circuit for the CMOS op amp.

7.7.1 A Two-Stage CMOS Op Amp

How to remain constant g_m

Currents through Q12 & Q13 due to current mirror

$$I_B = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_{12} (V_{GS12} - V_t)^2 \quad (7.212)$$

$$I_B = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_{13} (V_{GS13} - V_t)^2 \quad (7.213)$$

Gate-source voltages at Q12 & Q13

$$V_{GS13} = V_{GS12} + I_B R_B$$

$$V_{GS13} - V_t = V_{GS12} - V_t + I_B R_B$$

$$\sqrt{\frac{2I_B}{\mu_n C_{ox} (W/L)_{13}}} = \sqrt{\frac{2I_B}{\mu_n C_{ox} (W/L)_{12}}} + I_B R_B \quad (7.214)$$

$$I_B = \frac{2}{\mu_n C_{ox} (W/L)_{12} R_B^2} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)^2 \quad (7.215)$$

$$I_B \propto \frac{1}{(W/L)_{12} R_B^2}$$

$$R_B = \frac{2}{\sqrt{2\mu_n C_{ox} (W/L)_{12} I_B}} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$g_{m12} = \sqrt{2\mu_n C_{ox} (W/L)_{12} I_B}$$

$$g_{m12} = \frac{2}{R_B} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right) \quad (7.216)$$

g_{m12} can be constant.
(determined only by R_B , ration of $(W/L)_{12}$ and $(W/L)_{13}$)

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \quad g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$