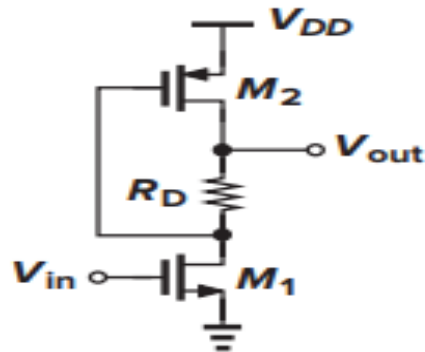


## ACMOS ECE315 / ECE515

### PRACTICE SHEET-2


**Q1)** Assuming all MOSFETs are in saturation, calculate the small-signal voltage gain of circuit in Fig. 1. ( $\lambda = 0$ ,  $\gamma = 0$ ) (**fig 1.**)



(fig 1.)


**Q2)** In the cascode stage of Fig. 2, assume that  $(W/L)_1 = 50/0.5$ ,  $(W/L)_2 = 10/0.5$ ,  $I_{D1} = I_{D2} = 0.5$  mA, and  $R_D = 1$  k.  $V_{th} = 0.77$  V. Ignore Body effect. (**fig 2.**)

- (a) Choose  $V_b$  such that  $M_1$  is 50 mV away from the triode region.
- (b) Calculate the small-signal voltage gain.

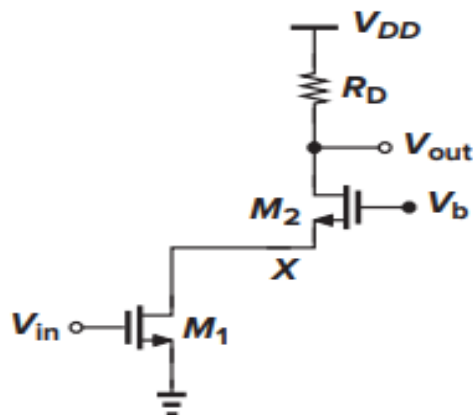


(fig 2.)

- Q3)** Assuming all the MOSFETs in Fig. 3 are in saturation and  $\lambda = 0$ ,  $\gamma = 0$ ,  
 (a) draw a simplified small-signal equivalent model of the circuit in Fig 3.  
 (b) calculate the small-signal voltage gain of the circuit. **(fig 3.)**

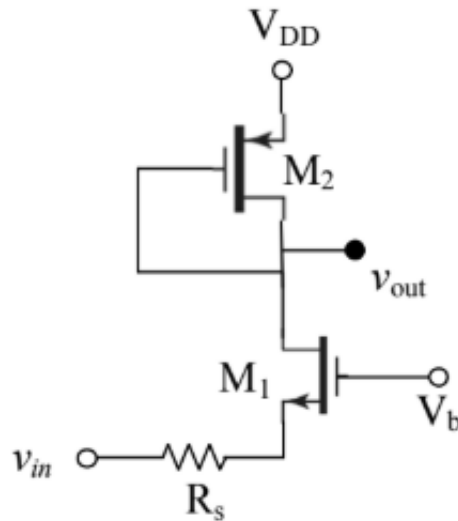


**(fig 3.)**

- Q4)** Two identical NMOS transistors are used as constant current sources in a system Fig. 4. However, due to the internal circuitry of the system,  $V_X$  is higher than  $V_Y$  by  $V$ .  
 (a) Calculate the resulting difference between  $I_{D1}$  and  $I_{D2}$  if  $\lambda = 0$ . **(fig 4.)**

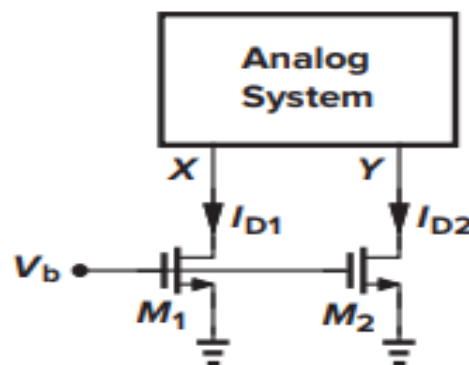

**(fig 4.)**

**Q5)**What will be the voltage at node Vout for the following circuit?( $V_{th}$  for all NMOS is 1V). **(fig 5.)**

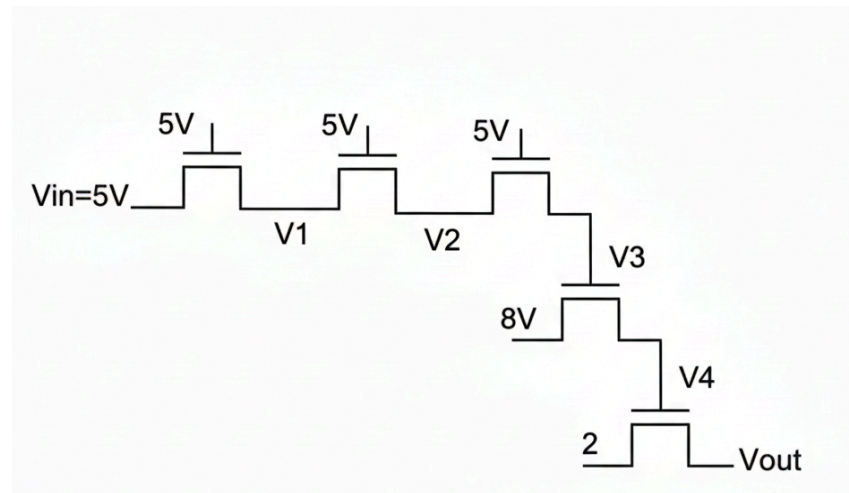

**(fig 5.)**