

VLSI Design Flow

Solution of Mid Semester Exam (27th September 2025)

Time allowed: 1 hour

Maximum Marks: 30

1.

a.

- i. Photoresist
- ii. Etching

[0.5X2=1 Mark]

- b. Number of good dies on one wafer = $400 \times 75 / 100 = 300$
Number of wafer need processing = $300000 / 300 = 1000$

[1+1 Marks]

c.

- i. OPC (optical proximity correction)
- ii. Multi-patterning/double patterning

[0.5X2=1 Mark]

d.

- i. High-level Synthesis, HLS, Behavior Synthesis
- ii. Hardware-software partitioning
- iii. Technology mapping or mapping
- iv. Power Planning or Chip Planning
- v. Detailed Routing or Routing
- vi. Engineering Change Order or ECO


[0.5X6=3 Marks]

- e. a=0 b=1

[1+1 Marks]

2.

a.

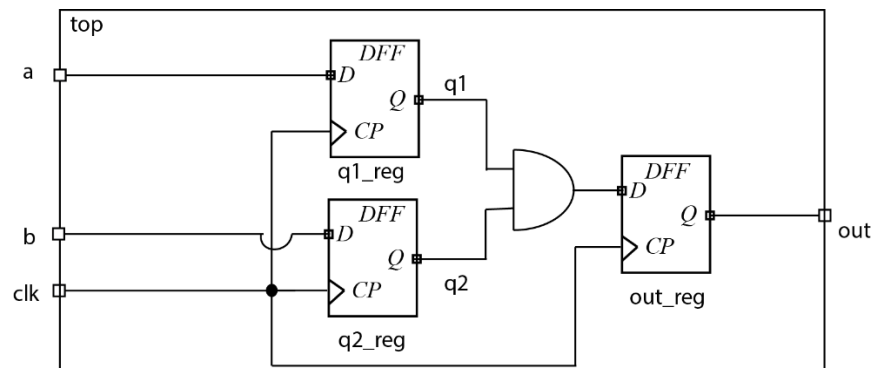


1 Marks for correct port and module names. (-0.2 for missing or wrong port name)

0.5*3=1.5 Marks for each flip-flop with correct connection of D, Q and CP (If anything is wrong for a flip-flop, no marks for that flip-flop)

1.5 if rest is correct (0 otherwise, no step-marking here)

b.

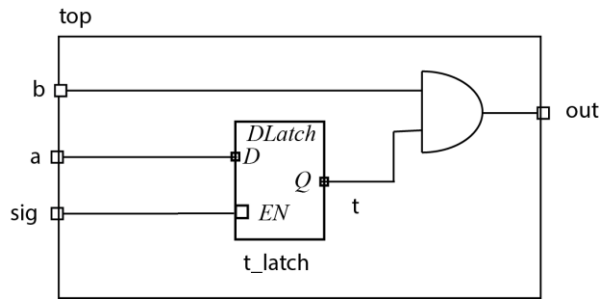

1 Marks for correct port and module names (-0.2 for missing or wrong port name)

1 Marks for latch with correct connection of D, Q and EN (If anything is wrong for the latch, no marks for the latch)

1 if rest is correct (0 otherwise, no step-marking here)

3.

- a. 10% to 90% threshold corresponds to 0.8 fraction of the linear ramp.

Hence,

Slew at D = $0.8 \times 30 = 24$ ps [1 Mark]

Slew at CP = $0.8 \times 10 = 8$ ps [1 Marks]

From the library data, setup time for slew of 24 ps at D and slew of 8 ps at CP = 45 ps [1 Mark]

- b. From the library data, clock-to-Q delay for slew of 8 ps at CP and load of 20 ff = 35 ps [2 Marks]

4.

For path from F1 to F2 for hold:

AT = 30 ps

RT = $20 + 20 + 10 = 50$ ps

Slack = $30 - 50 = -20$ ps [1+1+1 Marks]

No step marking for the numbers. If anything wrong in AT, RT, Slack: 0 is awarded

5.

- a. For path from F1 to F2 for setup longest data path should be considered:

AT = $40 + 100 + 50 + 100 = 290$ ps

RT = $1000 - 35 = 965$ ps

Slack = $965 - 290 = 675$ ps [1+1+1 Marks]

- b. For path from F1 to F2 for hold shortest data path should be considered:

AT = $40 + 100 + 100 = 240$ ps

RT = 25 ps

Slack = $240 - 25 = 215$ ps [1+1+1 Marks]

No step marking for the numbers. If anything wrong in AT, RT, Slack: 0 is awarded