

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING  
INDRAPRASTHA INSTITUTE OF INFORMATION TECHNOLOGY DELHI

MONSOON Semester

ECE 315/ ECE515: Analog CMOS Circuit Design

2023 – 2024

**Time: 2 hours**

**End-Semester Exam**

**M.M.: 30**

**Instructions:** All questions carry sufficient information. **No further information will be provided during the exam.** Please answer all parts of the same question together at the same place, not here and there.

1. For the circuit shown in Fig. 1,  $V_{DD} = 1.8 \text{ V}$ ,  $R_D = 500 \Omega$  and transistor  $M_1$  is characterized by the following parameters:  $\mu C_{ox} = 200 \mu\text{A/V}^2$ ,  $V_{TH} = 0.4 \text{ V}$ ,  $\lambda = 0$ ,  $\gamma = 0$ . The circuit provides an input impedance of  $50 \Omega$ .
- (a) What is the output resistance of the circuit? [1+1+2+1]
- (b) What is the value of maximum allowable of drain current?
- (c) Calculate the required value of  $W/L$  for the maximum allowable value of drain current. (1 mark if only  $g_m$  is correct, full marks if  $W/L$  is correct)
- (d) Compute the voltage gain.

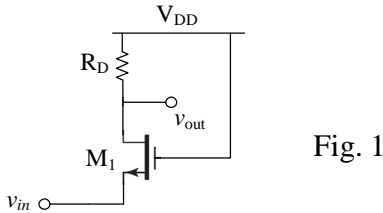


Fig. 1

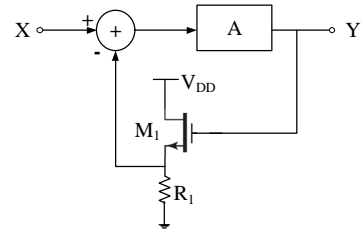


Fig. 2

2. (a) Find the loop-gain of the circuit shown in Fig. 2 where A is given as open-loop gain. Assume  $\lambda = 0$ ,  $\gamma = 0$  for  $M_1$ .
- (b) Find the small signal gain of the amplifier shown in Fig. 3. Assume  $\lambda \neq 0$ ,  $\gamma = 0$  and  $g_m r_o \gg 1$  for all the transistors.
- (a) if sign of the open loop gain is wrong, reduce 0.5 mark [2+3]
- (b) If any of the  $R_{out}$  upper or  $R_{out}$  lower is correct, 1.5 marks.

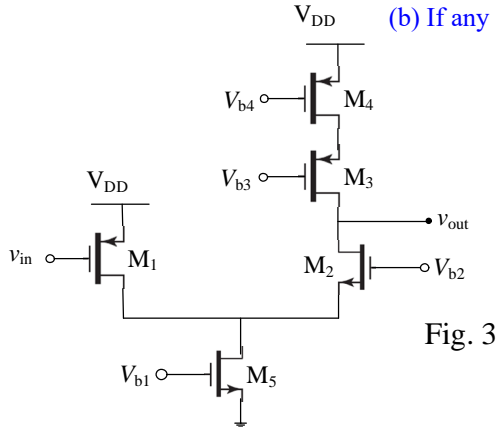


Fig. 3

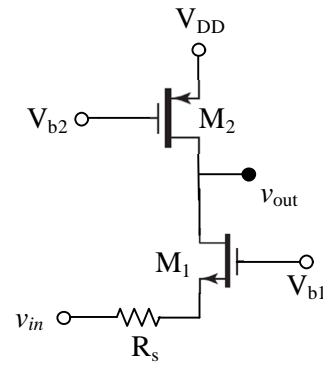


Fig. 4

3. Let us assume that the circuit in Fig. 4 is given for frequency response analysis.
- (a) Identify the capacitors, which experience Miller effect, if there is any. (a) Full 2 marks for correct identification [2+3]
- (b) Identify the poles by inspection. Assume  $\lambda = 0$ ,  $\gamma = 0$  for  $M_1$ ,  $\lambda \neq 0$ ,  $\gamma = 0$  for  $M_2$  and  $g_m r_o \gg 1$  for all MOS devices. (b) 1.5 marks for each correct pole.
4. (a) What are the usual bias conditions for the NMOS device shown in Fig. 5 to operate in deep triode region?
- (b) Neglecting all other capacitances, find the output impedance of the circuit shown in Fig. 6. Assume  $\lambda = 0$ ,  $\gamma = 0$  for the transistor and  $I_S$  is an ideal current source. [1+2+2]

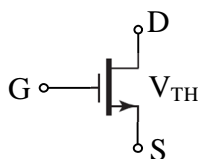


Fig. 5

$V_{DS} \ll 2(V_{GS} - V_{TH})$  -- 0.5marks  
and  $V_{GS} > V_{TH}$  ----- 0.5 marks

 


Fig. 6

(b) If any of the KCL or KVL equation is correct, 1 mark

(c) Full 2 marks if model is correct with proper labeling

(c) Draw the small-signal equivalent model for the circuit shown in Fig. 7 with proper labeling. Assume  $\lambda \neq 0$  and  $\gamma = 0$  for both the transistors.

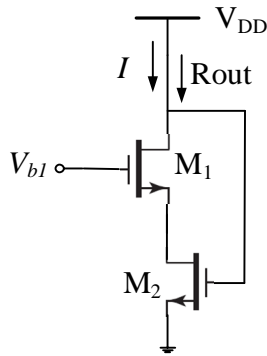


Fig. 7

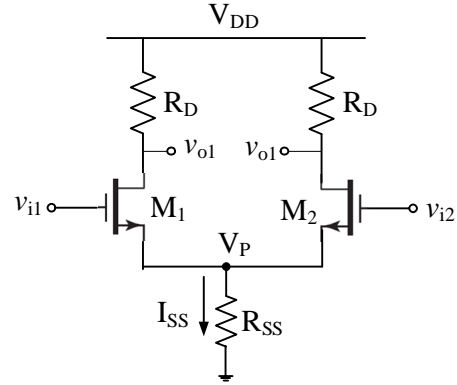


Fig. 8

5. For the circuit shown in Fig. 8,  $V_{DD} = 3 \text{ V}$ ,  $R_{SS} = 500 \Omega$ ,  $(W/L)_{1,2} = 25/0.5$ ,  $(\mu C_{ox})_{1,2} = 50 \mu\text{A}/\text{V}^2$ ,  $V_{TH1,2} = 0.6 \text{ V}$ . Assume  $\lambda = 0$ ,  $\gamma = 0$  for all the MOS devices. [2+2+1]

(a) What is the required input CM voltage for which  $V_P$  can be at least  $0.5 \text{ V}$ ? If only  $I_D$  is correct, 1 mark

(b) Calculate  $R_D$  for which the differential mode gain is 4. If  $R_{SS}$  is also taken into account in gain formula, full 2 marks

(c) Calculate the amount of voltage the transistors are away from entering the triode region.

6. (a) Calculate the output resistance ( $R_{out}$ ) denoted in the circuit of Fig 7. Assume  $\lambda \neq 0$  and  $\gamma = 0$  for both the transistors. There are two KCL equations is correct, 1 mark [2+1+2]

(b) Give just one disadvantage of having large voltage headroom in a MOS circuit.

(c) Assume all MOS devices in Fig. 9 are identical having threshold voltage  $V_{TH}$ , and  $\lambda = 0$ ,  $\gamma = 0$  for all of them. Find minimum allowable voltage at node P of the circuit to operate all the transistors in saturation.

$$V_P = V_{GSO} + V_{GS1} - V_{TH}$$

$$\text{or } V_P = (V_{GS0} - V_{TH}) + (V_{GS1} - V_{TH}) + V_{TH}$$

Full marks for both the forms.

 


Fig. 9