

Digital VLSI Design (ECE 314/514)
End-Sem Examination
5-Dec-2023


Duration: 2 hr

MM: 30 marks/ 28 marks (for B.Tech)

Q.1.a) Why does a FF need to satisfy setup time and hold time constraints? Explain in detail. **[1 mark]** [CO4]

b) Suppose you have designed a chip, and after fabrication, it fails. How would you determine if it is a setup failure or a hold time failure? **[1 mark]** [CO4]

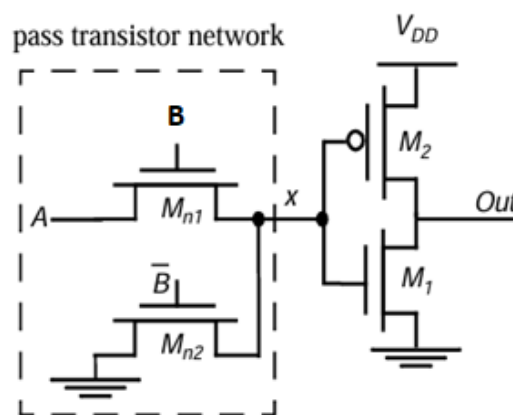Q2. Consider the circuit as shown below. Assume the inverter switches at $V_{DD}/2$, neglect body effect, channel length modulation, and all parasitic capacitance throughout this problem.



- What is the logic function performed by this circuit? **[1 mark]** [CO4]
- Explain why this circuit has non-zero static dissipation. **[1 mark]** [CO4]
- Using only just 1 transistor, design a fix so that there will not be any static power dissipation. Explain the constraints that you would consider when sizing this transistor. **[2 marks]** [CO4]

Q3. Answer the following questions.


- Draw the schematic of a 2-input domino AND gate. **[1 mark]** [CO4]
- If one engineer removed the footer nmos from the gate in part (a), how does this impact the delays compared to the original gate? **[1 mark]** [CO4]
- Are there any failure modes? Please explain. **[1 mark]** [CO4]

Q.4. Answer the following questions


- What is sequencing overhead? **[1 mark]** [CO4]
- What is adaptive sequencing? Describe any 2 adaptive sequencing methods in brief. **[3 marks]** [CO4]

Q. 5. The minimum and maximum delays through the logic are annotated on the figure, and the flip-flops have the following properties: $t_{cq} = 50\text{ps}$, $t_{\text{setup}} = 50\text{ps}$, and $t_{\text{hold}} = 50\text{ps}$. You can assume that the clock has no jitter.

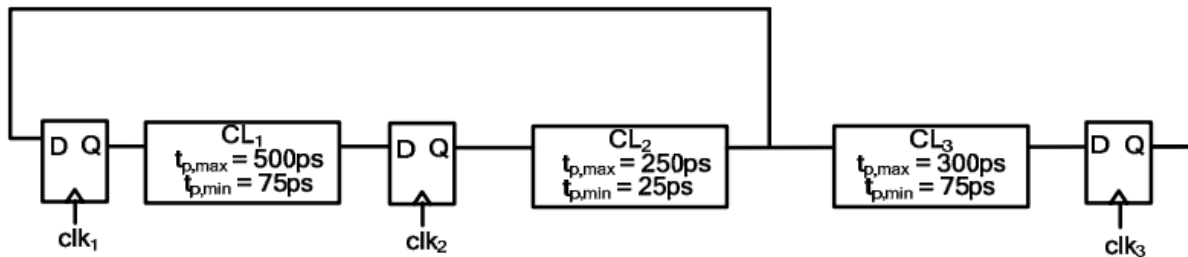a) Assuming there is no skew between clk_1 , clk_2 , and clk_3 , list all the timing constraint paths; what is the minimum clock cycle time for this pipeline? Are there any minimum delay (hold time) violations? **[3 marks]** [CO4]



 
b) Now, we'll include the clock distribution network for this pipeline. Assuming that the delay of each inverter is nominally 50ps, what is the minimum clock cycle time? **[2 marks]** [CO4]



Q6. Answer any 4 of the following questions. If all parts are answered, then it will be considered 'bonus' **[4 x 1 marks + 2 x 1 marks bonus]** [CO5]


- Why are non-volatile memories called non-volatile?
- Give two examples of Non-Random Access Memory.
- Which type of memory should be preferred if very high-speed access is the most important requirement?
- Why are Flash memories denser than SRAMs?
- Why are SRAMs better than Flash in terms of endurance?
- Why are Design rules for layout allowed to be violated in SRAM array design?

 Q7. a) Determine the activity factor at each node in the circuit, assuming the input probabilities $P_a = P_b = P_c = P_d = 0.5$. **[3 marks]** [CO3]



b) The circuit above (part-a) sees a total load capacitance of 10fF and is operated at 0.6V. The time period of the system clock is 2ns. Find the switching power of the circuit. **[1 mark]** [CO3]

 Q8 .a) i) Calculate the maximum operational frequency of the following circuit. **[1 mark]** [CO4]



ii) Calculate the setup slack if the clock period is 2ns. **[1 mark]** [CO4]

b) If the 2nd FF is replaced with a negative edge-triggered FF, Calculate the maximum operating frequency. Assume same timing parameters. **[bonus for B.Tech students]** **[2 marks]** [CO4]

